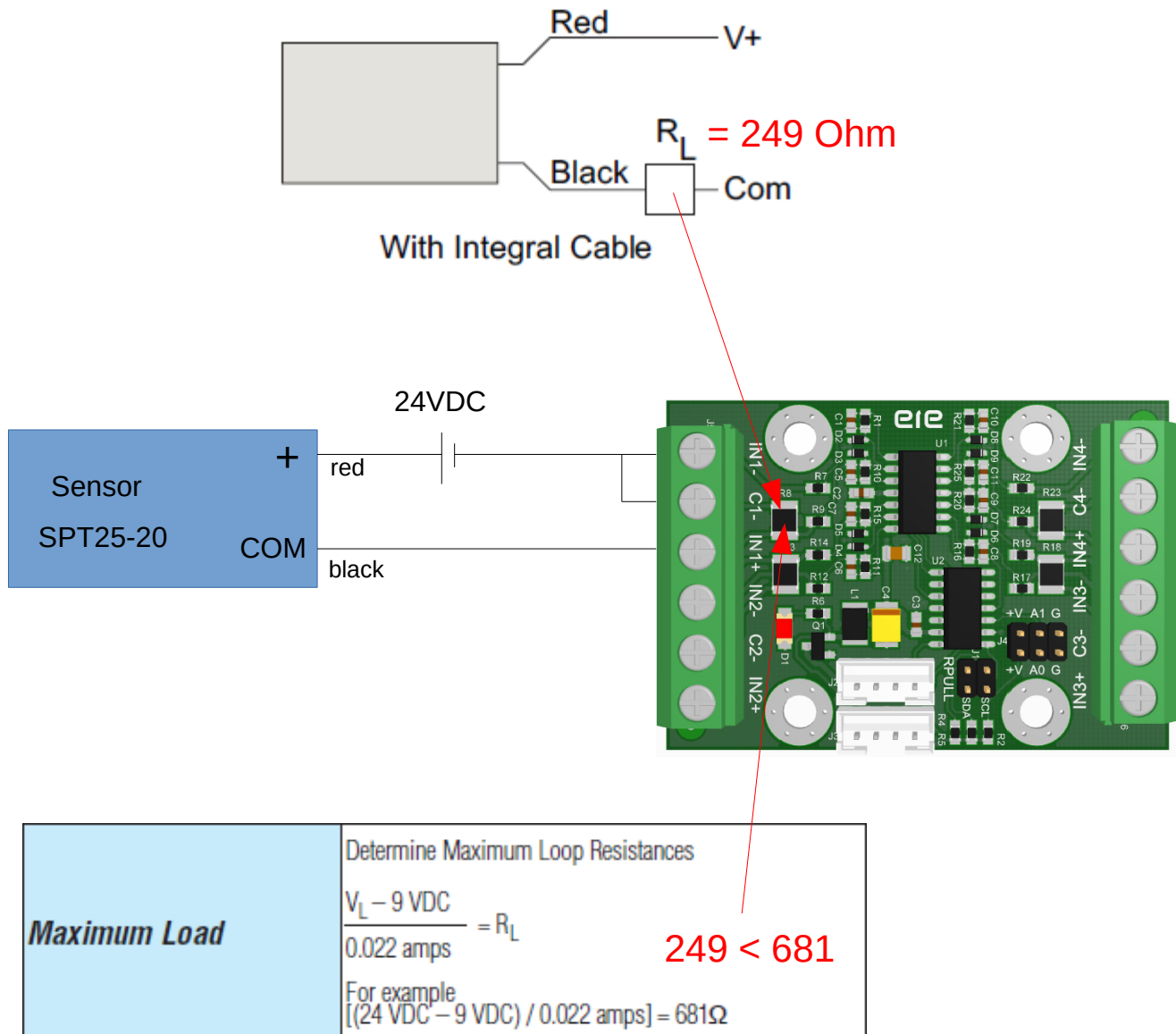


I2C-AI418S Application

Connection with 2-wire 4-20mA SPT25-20



The I2C-AI418S has already had R_L in each input channel. So you don't need to have external R_L . You can use the R_L on the I2C-AI418S. The R_L on the I2C-AI418S is 249 ohm which this value is less than the maximum load of the sensor, SPT25-20 when you use 24VDC power supply.



ERE Company Limited.

www.ereshop.com